



**L-Università  
ta' Malta**

MATRICULATION AND SECONDARY EDUCATION CERTIFICATE  
EXAMINATIONS BOARD

**SECONDARY EDUCATION CERTIFICATE LEVEL  
2026 MAIN SESSION**

---

SUBJECT:	<b>Engineering Technology</b>
PAPER NUMBER:	Controlled – Unit 2
DATE:	6 <sup>th</sup> May 2025
TIME:	10:00 a.m. to 11:35 a.m.

---

**THIS PAPER SHOULD BE RETURNED TO THE INVIGILATOR  
AFTER THE EXAMINATION.**

**Name of candidate** \_\_\_\_\_

**I.D. number** \_\_\_\_\_

**School** \_\_\_\_\_

**Class** \_\_\_\_\_

Answer **ALL** questions in the space provided. The use of non-programmable electronic calculators is allowed.

### Scenario

Candidates for an electronics technician apprenticeship post were asked to sit for the following test to verify their knowledge and competences.

### Question 1

**K-1 (4 marks)**

Materials can be categorised into three main groups: conductors, semiconductors, and insulators.

- a. Categorise the different materials provided below as conductors or insulators in the appropriate column of Table 1. An example for each category is provided to help you.

Paper	Iron	Rubber	Brass
-------	------	--------	-------

Table 1: Conductors and Insulators

Conductor	Insulator
Copper	Oil

(1)

- b. Define the term semi-conductor.

---



---



---



---

(1)

- c. The resistance of a copper wire depends on different parameters. State any **TWO** of these parameters.

---



---



---



---

(2)

**Question 2****K-3 (4 marks)**

- An electrical circuit can either be closed or open.
- Electrical circuits can either be series, parallel or a combination of the two.

a. Differentiate between an open and a closed circuit.

---

---

---

---

(1)

b. In the space provided below draw:

- i. A series circuit consisting of a 1.5 V battery and two resistors one of  $270\ \Omega$  and the other of  $620\ \Omega$ .

(0.5)

- ii. A parallel circuit made up of a 1.5 V battery and a  $220\ \Omega$  resistor in parallel with a  $300\ \Omega$  resistor.

(0.5)

***This question continues on next page.***

c. A series-parallel circuit is shown in Figure 1.

Identify **ONE** series and **ONE** parallel circuit combination by referring to the resistors R1, R2 and R3. Write your answers in the space provided below.

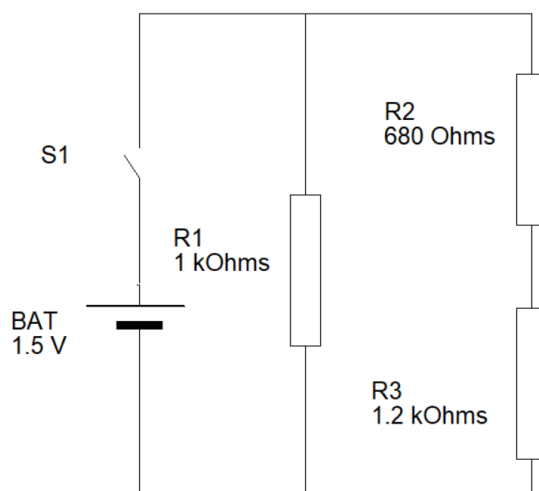


Figure 1: Series-parallel circuit

Series sub-circuit: \_\_\_\_\_ (1)

Parallel sub-circuit: \_\_\_\_\_ (1)

### Question 3

**C-2 (6 marks)**

The power supplied by a battery can be calculated using the equivalent resistance of a circuit.

a. Find the total resistance of the circuit shown in Figure 2. Show all your working.

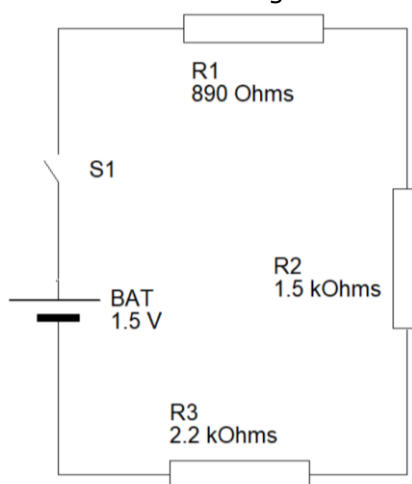


Figure 2: Circuit 1

---



---



---





**Question 4****C-3 (6 marks)**

The required equivalent capacitance is necessary to determine the total charge supplied by the battery.

- a. Find the total capacitance of the circuit shown in Figure 5 below. Show all your working.

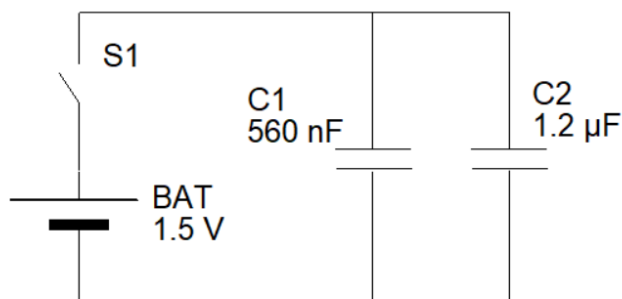


Figure 5: Circuit 4

---



---



---



---

(2)

- b. Find the total capacitance of the circuit shown in Figure 6 below. Show all your working.

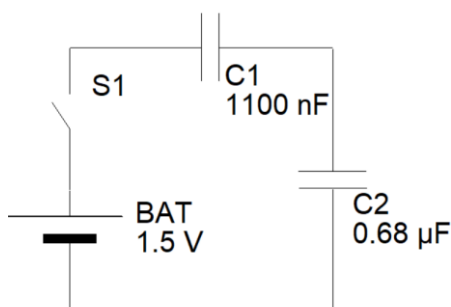


Figure 6: Circuit 5

---



---



---



---



---



---

(2)

***This question continues on next page.***

- c. For the RC circuit shown in Figure 7, find the resistance value of resistor R1 to achieve a time constant of 5.28s.

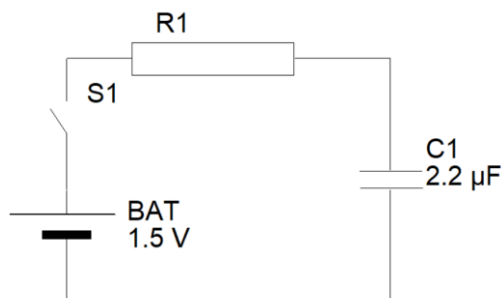


Figure 7: Circuit 6

(2)





### Question 5

**K-6 (4 marks)**

A signal waveform defines the changes of a parameter as a function of time.

a. Identify the **TWO** different signals tabulated in Table 2.

Table 2: Different types of Signals

	Signal	Name
i.		<div></div> <div>(0.5)</div>
ii.		<div></div> <div>(0.5)</div>

(Source: <https://www.analog.com>)

b. Define **TWO** parameters of a sine wave signal, and their SI units.

Parameter 1: \_\_\_\_\_

SI Unit of Parameter 1: \_\_\_\_\_ (0.5)

Parameter 2: \_\_\_\_\_

SI Unit of Parameter 2: \_\_\_\_\_ (0.5)

***This question continues on next page.***

c. Label the important features of the oscilloscope shown in Figure 8.

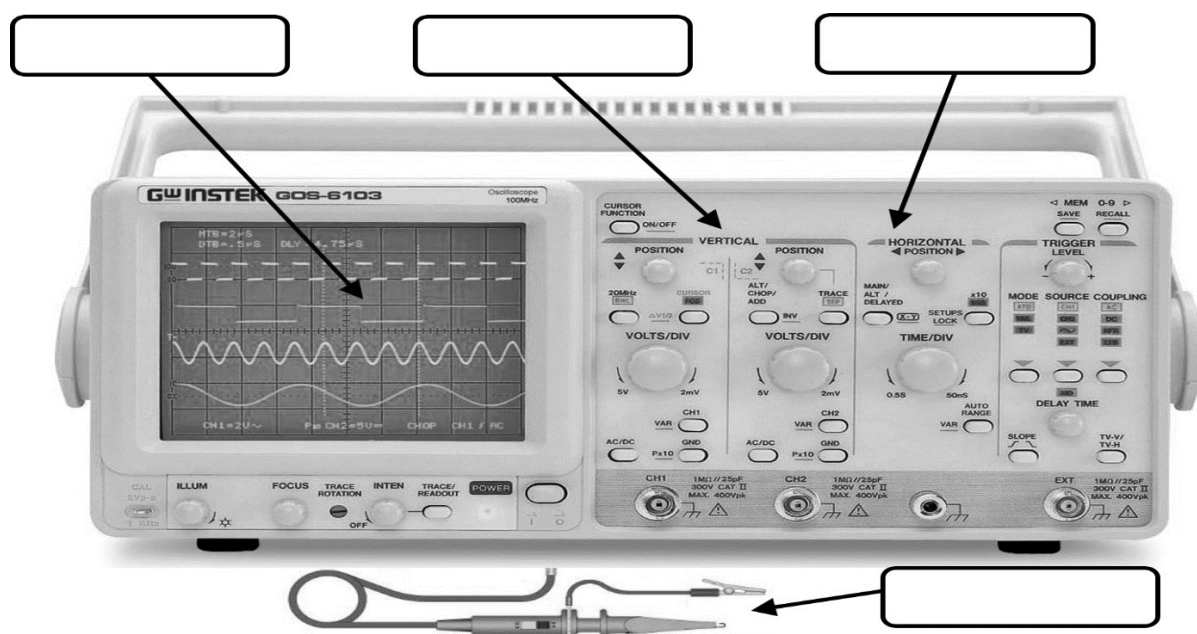


Figure 8: Oscilloscope  
(Source: <https://www.techedu.org/>)

(2)





### Question 6

**K-9 (4 marks)**

Electronic components can be represented using standardised symbols.

a. Identify all the electronic symbols illustrated in Table 3.

Table 3: Electronic Symbols.

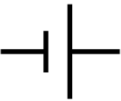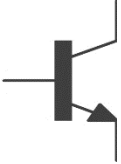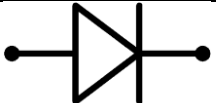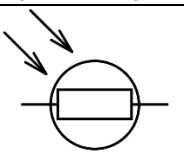	Electronic Symbol	Name
i.	 (Source: <a href="https://www.iso.org/">https://www.iso.org/</a> )	_____ (0.25)
ii.	 (Source: <a href="https://learn.sparkfun.com/">https://learn.sparkfun.com/</a> )	_____ (0.25)
iii.	 (Source: <a href="https://www.petervis.com/">https://www.petervis.com/</a> )	_____ (0.25)
iv.	 (Source: <a href="https://electronics.stackexchange.com/">https://electronics.stackexchange.com/</a> )	_____ (0.25)

- b. Match the given SI units on the left to their respective parameters on the right by connecting a line between them.



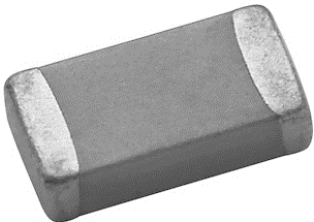

Farads
Watts
Volts
Ohms

Resistance
Capacitance
Voltage
Power

(1)

- c. Table 4 below shows different packaging for a resistor and a capacitor. Identify each of the given package, by underlining the correct answer.

Table 4: Component Packaging.

	Component	Packaging 1	Packaging 2
i.	Resistor	 Radial / Axial	 Radial / Axial
ii.	Capacitor	 Through hole / Surface mount	 Through hole / Surface mount

(Sources: <https://forum.digikey.com>, <https://www.ie.farnell.com>,  
<https://www.vishay.com/>, <https://www.flyrobo.in>)

(2)





**Please turn the page.**

**Question 7****K-10 (4 marks)**

Specialised and well-kept tools are essential to construct good quality electronic circuits.

a. Label the different tools used in the construction of electronic circuits shown in Table 5.

Table 5: Tools

	<b>Tool</b>	<b>Name</b>
i.	 <p>(Source: <a href="https://www.gedore.com/">https://www.gedore.com/</a>)</p>	_____ (0.25)
ii.	 <p>(Source: <a href="https://www.toptul.com/">https://www.toptul.com/</a>)</p>	_____ (0.25)
iii.	 <p>(Source: <a href="https://mecha-tronx.com/">https:// mecha-tronx.com/</a>)</p>	_____ (0.25)
iv.	 <p>(Source: <a href="https://au.rs-online.com/">https:// au.rs-online.com/</a>)</p>	_____ (0.25)

- b. Identify the missing **FOUR** steps in the correct order to use a soldering iron effectively. The final step has already been provided.

Step 1: \_\_\_\_\_ (0.25)

Step 2: \_\_\_\_\_ (0.25)

Step 3: \_\_\_\_\_ (0.25)

Step 4: \_\_\_\_\_ (0.25)

Step 5: Allow the solder joint to solidify appropriately.

- c. PCB circuit construction requires different tools with different functions. Outline the functions of the following **TWO** tools used in a circuit construction.

De-Soldering Pump	Track Cutter
-------------------	--------------

[illegible]





***Please turn the page.***

**Question 8****C-5 (6 marks)**

The PCB manufacturing process present a number of hazards which are mitigated with different safety precautions.

- a. Identify the appropriate warning sign for each of the hazardous scenarios listed in Table 6. Draw a circle around the correct sign.

Table 6: Warning signs for hazardous scenarios.

	Scenario	Warning Sign
i.	A liquid used during the etching process that creates oxidation	 
ii.	A liquid used during the etching process that is hazardous to the environment	 

(1)

(1)

(Source: <https://www.vectorstock.com/>, <https://depositphotos.com/>, <https://www.vecteezy.com/>)

- b. Identify **FOUR** hazards from the ones provided below that might be present when manufacturing a PCB.

Inhaling dangerous fumes	Cuts	Inadequate lighting
Low solder iron tip temperature	Chemical spill	Airborne fragments

Hazard 1: \_\_\_\_\_ (0.5)

Hazard 2: \_\_\_\_\_ (0.5)

Hazard 3: \_\_\_\_\_ (0.5)

Hazard 4: \_\_\_\_\_ (0.5)

c. Identify **FOUR** ways to eliminate or minimize the risks involved when manufacturing a PCB.

Use of sub-standard material	Safe waste disposal
Safe handling of chemicals	Overlooking PCB design rules
Regular equipment maintenance	Wear appropriate PPE

Minimize risk 1: \_\_\_\_\_ (0.5)

Minimize risk 2: \_\_\_\_\_ (0.5)

Minimize risk 3: \_\_\_\_\_ (0.5)

Minimize risk 4: \_\_\_\_\_ (0.5)

# Blank Page